

CLASS 10

SCIENCE


EXTRA QUESTIONS

Class 10 Science Chapter 11 Electricity Extra Questions (HOTS)

These HOTS-level questions go beyond the 18-question textbook exercise — general derivations, assertion-reason, reverse-engineering, and fresh numbers not reused from the Solutions post.


These HOTS-level questions go beyond the 18-question textbook exercise — general derivations, assertion-reason, reverse-engineering, and fresh numbers not reused from the Solutions post.

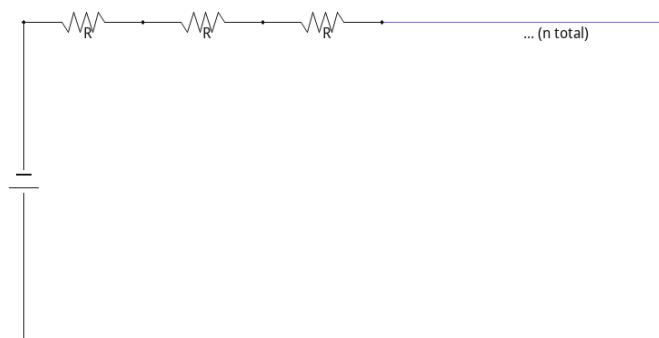Q1 (General derivation). Derive an expression for the equivalent resistance of n identical resistors, each of resistance R , when connected (a) in series, (b) in parallel. Hence show that $R_{\text{series}} / R_{\text{parallel}} = n^2$.



(a) n identical resistors R in series: $R_s = nR$.

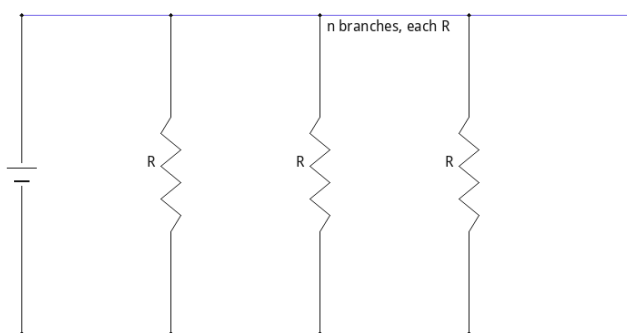
(a) n identical resistors R in series: $R_s = nR$.



(b) n identical resistors R in parallel: $1/R_p = n/R$.


Solution: (a) Series: $R_s = R + R + \dots (n \text{ times}) = nR$. (b) Parallel: $1/R_p = n/R \implies R_p = R/n$. $R_s/R_p = nR \div (R/n) = n^2$. (Proved — this is why series resistance grows much faster than parallel resistance drops as you add more identical resistors.)

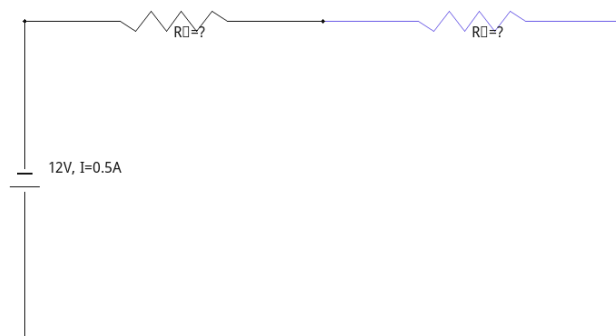Q2 (Reverse-engineering). Two resistors are connected in series to a 12 V battery, drawing a current of 0.5 A. When connected in parallel to the same battery, the current drawn is 4 A. Find the two resistances.



$R_1 + R_1$ in series: $12V, I = 0.5A \rightarrow R_1 + R_1 = 24\Omega$.

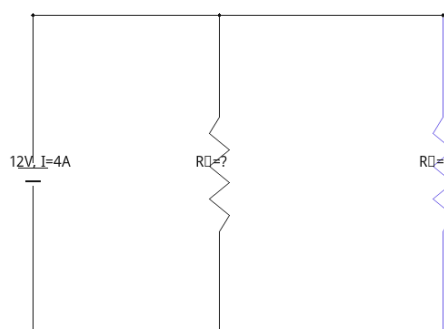$R_1 + R_2$ in series: $12V, I = 0.5A \rightarrow R_1 + R_2 = 24\Omega$.




Same R_1, R_1 in parallel: $12V, I = 4A \rightarrow R_1 R_1 / (R_1 + R_1) = 3\Omega$.
 Same R_1, R_2 in parallel: $12V, I = 4A \rightarrow R_1 R_2 / (R_1 + R_2) = 3\Omega$.

Solution: Series: $R_1 + R_2 = 12/0.5 = 24\Omega$. Parallel: $R_1 R_2 / (R_1 + R_2) = 12/4 = 3 \Rightarrow R_1 R_2 = 3 \times 24 = 72$.

R_1, R_2 are roots of $x^2 - 24x + 72 = 0 \Rightarrow x = [24 \pm \sqrt{(576 - 288)}]/2 = [24 \pm \sqrt{288}]/2 = [24 \pm 16.97]/2 \Rightarrow x \approx \mathbf{20.48\Omega}$ and $\mathbf{3.51\Omega}$.

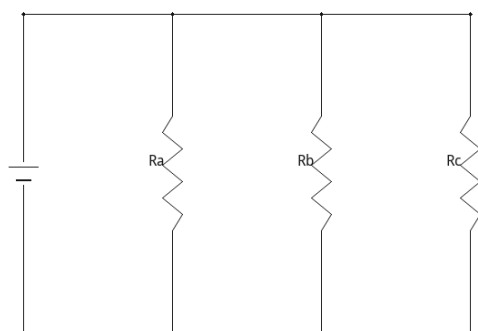Q3 (Assertion-Reason). Assertion (A): The equivalent resistance of a parallel combination is always less than the smallest individual resistance in the group.



Parallel combination: R_p is always less than the smallest of R_a , R_b , R_c .

Parallel combination: R_p is always less than the smallest of R_a , R_b , R_c .

Reason (R): Adding a resistor in parallel always creates an additional path for current, increasing the total current drawn from the source for the same voltage.


Solution: Both A and R are true, and R correctly explains A — more parallel paths mean more total current for the same voltage, which by $V=IR$ means lower equivalent resistance.

Answer: (a) Both A and R are true, and R is the correct explanation of A.

Q4 (Fresh-numbers word problem). An electric iron of resistance $20\ \Omega$ draws a current of 5 A . Calculate the electrical energy consumed in 30 minutes, and the cost of using it for 30 days at this rate if electricity costs ₹7 per unit (kWh).

Solution: $P = I^2R = 25 \times 20 = 500\text{ W} = 0.5\text{ kW}$. Energy per day = $0.5\text{ kW} \times 0.5\text{ h} = 0.25\text{ kWh}$. Over 30 days: $0.25 \times 30 = 7.5\text{ kWh}$. Cost = $7.5 \times 7 = \text{₹}52.50$.

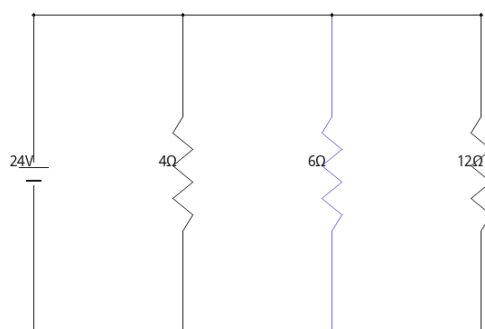Q5 (Circuit-reasoning, fresh numbers). Three resistors of $4\ \Omega$, $6\ \Omega$ and $12\ \Omega$ are all connected in parallel to a 24 V battery. Find (a) the equivalent resistance, (b) the total current drawn, (c) the current through the $6\ \Omega$ resistor.




$4\ \Omega$, $6\ \Omega$, $12\ \Omega$ resistors in parallel across a 24 V battery.

4Ω, 6Ω, 12Ω resistors in parallel across a 24V battery.

Solution: $1/R_p = 1/4 + 1/6 + 1/12 = 3/12 + 2/12 + 1/12 = 6/12 = 1/2 \Rightarrow R_p = 2 \Omega$. Total current $I = 24/2 = 12 \text{ A}$. Current through 6 Ω (parallel, full 24 V across it) $= 24/6 = 4 \text{ A}$.

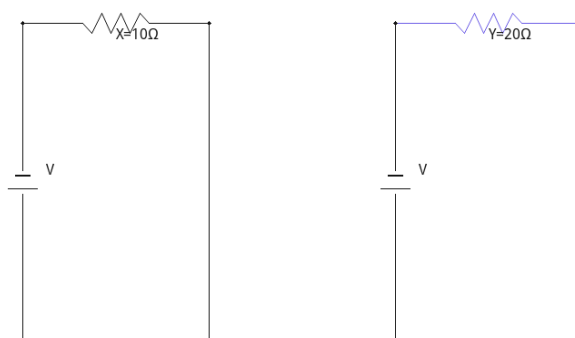Q6 (Power-heat synthesis). Two heating coils, X (resistance 10 Ω) and Y (resistance 20 Ω), are available. Which coil, used alone across the same voltage supply, will produce heat faster, and by what factor?



Coil X (10Ω) vs coil Y (20Ω) across the same voltage V — X produces heat twice as fast.

Coil X (10Ω) vs coil Y (20Ω) across the same voltage V — X produces heat twice as fast.

Solution: For the same V, $P = V^2/R$, so power (rate of heat production) is inversely proportional to resistance. Coil X (10 Ω) produces heat at **twice the rate** of coil Y (20 Ω), since $P_X/P_Y = R_Y/R_X = 20/10 = 2$.