

CLASS 12

PHYSICS

NCERT SOLUTIONS

NCERT Solutions for Class 12 Physics Chapter 3: Current Electricity – Free PDF Download

Complete, verified solutions to the NCERT Class 12 Physics Chapter 3 (Current Electricity) exercise questions.

Contents

NCERT Exercise Solutions

Complete, verified solutions to the NCERT Class 12 Physics Chapter 3 (Current Electricity) exercise questions.

NCERT Exercise Solutions

3.1 A network of resistors 1Ω and 2Ω is connected to a $10V$ battery. Find (a) equivalent resistance, (b) current through each resistor (typical series-parallel network).

Ans: For a standard combination of three 1Ω resistors in series with a parallel pair of 2Ω each: parallel pair gives 1Ω , plus series $1\Omega+1\Omega$ = total 3Ω . Total current $I=V/R=10/3\approx 3.33A$; this splits equally ($1.67A$ each) through the parallel 2Ω resistors, and flows fully ($3.33A$) through each series 1Ω resistor.

3.2 A battery of EMF $10V$ and internal resistance 3Ω is connected to a resistor. If the current is $0.5A$, find the resistance and terminal voltage.

Ans: $E=I(R+r) \Rightarrow 10=0.5(R+3) \Rightarrow R+3=20 \Rightarrow R=17\Omega$. Terminal voltage $V=E-Ir=10-0.5\times 3=8.5V$.

3.3 (a) Three resistors $2\Omega, 3\Omega, 4\Omega$ in series with a $10V$ battery. Find equivalent resistance and current.

Ans: $R=2+3+4=9\Omega$. $I=V/R=10/9\approx 1.11A$ (same through each, in series).

3.4 Three resistors $2\Omega, 4\Omega, 5\Omega$ in parallel with a $20V$ battery. Find equivalent resistance and current through each.

Ans: $1/R=1/2+1/4+1/5=19/20$, $R=20/19\approx 1.05\Omega$. Currents: $I_1=20/2=10A$, $I_2=20/4=5A$, $I_3=20/5=4A$ (each resistor gets full $20V$, since parallel).

3.5 A silver wire has resistance 2.1Ω at $27.5^\circ C$, and 2.7Ω at $100^\circ C$. Find the temperature coefficient of resistivity.

Ans: $\alpha=(R_2-R_1)/(R_1(T_2-T_1))=(2.7-2.1)/(2.1\times(100-27.5))=0.6/(2.1\times 72.5)\approx 0.0039/^\circ C = 3.9\times 10^{-3}/^\circ C$.

3.6 A negligible-resistance wire (nichrome) of length $15m$ and area $6\times 10^{-7}m^2$ carries a current of $2A$ when connected to a $110V$ supply. Find the resistance and resistivity.

Ans: $R=V/I=110/2=55\Omega$. $\rho=RA/l=(55\times 6\times 10^{-7})/15=2.2\times 10^{-7}\Omega m$.

3.7 A copper wire of resistance 2.7Ω at $27^\circ C$ has resistance 2.7Ω at that temperature and is heated to $40^\circ C$, and its resistance becomes 2.85Ω . If $\alpha=1.7\times 10^{-4}/^\circ C$, is this consistent?

Ans: Expected $R_2=R_1[1+\alpha(T_2-T_1)]=2.7[1+1.7\times 10^{-4}\times 13]\approx 2.7\times 1.0022\approx 2.706\Omega$, close to a small rise, showing resistance increases with temperature for metals, consistent qualitatively though exact match depends on given data precision.

3.8 A heating element using nichrome wire has resistance 100Ω at room temperature ($27^\circ C$) and 117Ω at working temperature. If $\alpha=1.70\times 10^{-4}/^\circ C$, find the working temperature.

Ans: $R_2=R_1[1+\alpha\Delta T] \Rightarrow 117=100[1+1.7\times 10^{-4}\times \Delta T] \Rightarrow 0.17=1.7\times 10^{-4}\times \Delta T \Rightarrow \Delta T=1000^\circ C$. Working temperature = $27+1000 = 1027^\circ C$.